

Name: _____

Class: _____

Total Possible Marks: 16

Resistance and IV Characteristics



____ 1.
10



(a) Resistance is anything in the (b) circuit which (c) reduces the (d) flow of (e) current. It is measured in ohms. The current flowing through a (f) component depends upon the (g) potential difference across it and the resistance of the component itself.

The (h) greater the resistance of a component, then the (i) smaller the current flowing through it for a given potential (j) difference, factors all linked together in the expression:

$$V = IR$$

circuit
difference

component
smaller

potential
current


Resistance
flow

greater
reduces

- 6 2. The relationship between potential difference current and resistance is given by the expression:

$$V = I \times R$$

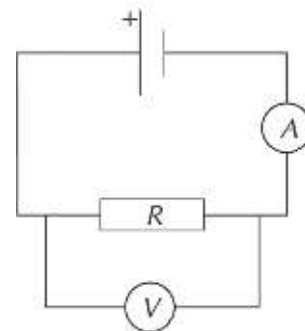Where V is the potential difference measured in volts, I is the current measured in amperes and R is a resistance measured in ohms.



* Allocate one mark for the calculation, that is the correct transposition of the equation and a 2nd mark for the correct answer

- 2 a. A voltmeter in a circuit across a resistor of resistance 4 ohms displays a reading of 6 V. An ammeter connected to the circuit would display what reading in amperes?

Given the expression above we know that $V = IR$ so by rearrangement $I = V / R$. Substituting known values of V and R:

$$I = 6 / 4 = 1.5 \text{ amperes}$$

- 2 b. The resistor is exchanged for another one, this time the ammeter reached 3 A, if the potential difference remains the same what is the resistance of the new component?

Using $V = IR$ and rearranging for $R = V / I$ we simply plug in the known values of 6 V and 3 A to reach a value of 2 ohms.

- 2 c. If we increase the potential difference by 100% and take a reading from the ammeter of 0.000025 A (25 micro amps) what is the resistance of the resistor component now?

Increasing the potential difference by 100% simply means doubling it to 12 V, using the expression $R = V / I$ and substituting our known values we arrive at a resistance of:

$$R = 12 / 0.000025 = 480,000 \text{ ohms which could also be written as } 480 \text{ k}\Omega \text{ or } 0.48 \text{ M}\Omega$$